

(1) read only -> برای انتقال دیتا به کار می رود. یعنی data در کنترل in:

output port: entity با کار می رود. این پورت می تواند write و read کند. یعنی out:

in out: entity با کار می رود و در حافظه data در

buffer: out است. در آن در entity می توان read و write کنیم. برای پورت می توانیم internal state در داخل entity مورد نیاز است.

linkage: خطی که اتصال می شود به physical بدنه یعنی ات دبی کنترل می باشد. اتصال می شود.

(2) ٤٧٨: binary: '11011110' octal: '736'

hexadecimal: 'IDE'

(3) identifier: نام های مستطرد همان های مختلف اشاره می کنند مثل architecture, entity

Variable, Constant, signal (برای ایجاد مولد از این ها می توانیم استفاده کنیم) identified (داریم)

وینی Case insensitive (مثلاً Alef = alef است) - کاراکترهای مجاز حروف - ارقام -

و نه: در تمام آن باید با حرف شروع شود. همچنین: (underscore) می تواند در انتهای کلمات

ع) هر یک برای ذخیره معادله‌های تعریف می‌شوند. در variable با معادله‌ای که assign می‌شود بلافاصله مقدار (در اعمال می‌شود)

اما signal با delay انجام می‌شود

- local variable: متغیری که خارج از block یا entity قابل دسترسی نیست اما signal یا process

های دیگر هم قابل دسترسی هستند برای communication بین قسمت‌های مختلف می‌تواند

- اگرچه در sensitivity list از تعریف signal، signal من است اما variable می‌تواند

- variable ما می‌توانیم sequential statement اما می‌توانیم concurrent

sequential تعریف می‌شود

- Persistence: variable با مقدار دهی آن را این در activation مختلف می‌تواند اما signal

ما مقدارشان را نمی‌توانیم در process یا cycle یا simulation

(5-1

1. Parameterizing Hardware Characteristics

Generics can be used to define key characteristics of hardware components, such as the width of data buses, memory size, or the number of interface ports. This allows a single entity design to be easily adapted for different hardware configurations.

Example:

```
entity FIFO_Buffer is
generic (
  DATA_WIDTH : integer := 8; -- Number of bits in data bus
  BUFFER_SIZE : integer := 64 -- Size of the FIFO buffer );
port ( ... );
end FIFO_Buffer;
```

2. Configuring Operational Parameters

Operational parameters like clock frequencies, timing constraints, or specific operational modes can be parameterized using generics. This enables the tuning of components for optimal performance in different environments.

Example:

```
entity Clock_Divider is
generic (
DIVIDE_BY : integer := 2; -- Factor by which to divide the input clock
); port ( ... );
end Clock_Divider;
```

3. Setting Initial Conditions

Generics can set initial conditions or default states for a design, such as initial values for registers or the default state for a state machine.

Example:

```
entity Counter is
generic (
INITIAL_VALUE : integer := 0; -- Initial value of the counter
); port ( ... );
end Counter;
```

4. Adapting to Different Technology Libraries

When targeting different FPGA or ASIC technology libraries, generics can be used to abstract differences in implementation details, such as logic cell configurations, making it easier to port VHDL code across platforms.

Example:

```
entity Generic_Adder is
generic (
TECH_LIBRARY : string := "ASIC_45nm" -- Target technology library
); port ( ... );
end Generic_Adder;
```

5. Feature Enablement and Experimental Configurations

Generics can enable or disable features of a component, such as debug modes, test features, or optional functionality. This allows a single design to be used in both development and production with different settings.

Example:

```
entity Processor is
generic (
DEBUG_MODE_ENABLED : boolean := false; -- Enable or disable debug mode
); port ( ... );
end Processor;
```

6. Simulation-Specific Parameters

For simulation purposes, generics can specify behaviors or parameters that are only relevant during simulation, such as simulating different operational conditions or hardware faults.

Example:

```
entity Sensor_Simulator is
generic (
FAULT_MODE : boolean := false; -- Simulate a fault condition );
port ( ... );
end Sensor_Simulator;
```

کد اصلاح شده آورده شده است و اشکالات به رنگ قرمز هستند:

entity Example is

```
Port (
    input_signal : in STD_LOGIC;
    output_signal : out STD_LOGIC
);
```

end Example ;

architecture Behavioral of Example is

```
signal internal_signal : STD_LOGIC;
```

```
begin
```

```
process
```

```
begin
```

```
if input_signal = '1' then
```

```
    internal_signal <= '1';
```

```
else
```

```
    internal_signal <= '0';
```

```
end if ;
```

```
end process;
```

```
output_signal <= internal_signal ;
```

end Behavioral ;

(سوال 2)

روند انجام : ابتدا در نرم افزار active hdl یک workspace ساخته و بعد یک فایل vhd. برای design اضافه می

کنیم. سپس کد مقایسه کننده

را در آن نوشته و کامپایل

می کنیم.


```
--entity declaration with port definitions
entity compare is
port(    num1 : in std_logic_vector(3 downto 0); --input 1
        num2 :    in std_logic_vector(3 downto 0); --input 2
        less :    out std_logic;    -- indicates first number is small
        equal :    out std_logic;    -- both are equal
        greater : out std_logic    -- indicates first number is bigger
);
end compare;

--architecture of entity
architecture Behavioral of compare is

begin
process(num1,num2)
begin
if (num1 > num2 ) then --checking whether num1 is greater than num2
less <= '0';
equal <= '0';
greater <= '1';
elsif (num1 < num2) then    --checking whether num1 is less than num2
less <= '1';
equal <= '0';
greater <= '0';
else    --checking whether num1 is equal to num2
less <= '0';
equal <= '1';
greater <= '0';
end if;
end process;

end Behavioral;
```

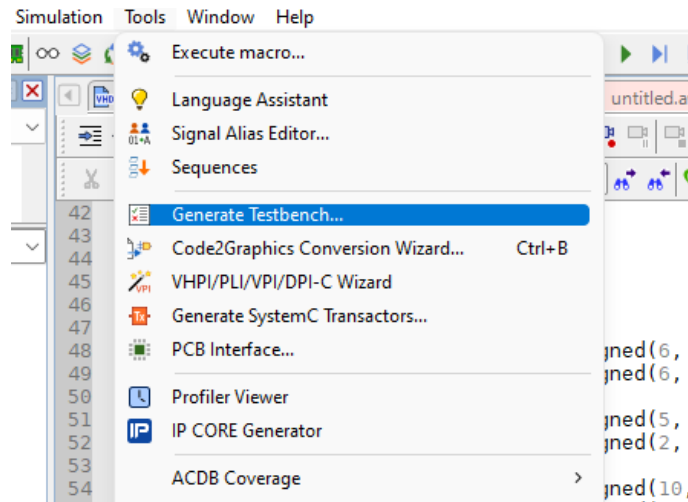سپس از قسمت generate testbench tools => برای آن فایل testbench ایجاد می کنیم




و بعد از اضافه کردن کد قسمت process آن waveform ایجاد می کنیم.

```
-- Add your stimulus here ...
process
begin
  wait for 20 ns;
  num1 <= std_logic_vector(to_unsigned(6, 4));
  num2 <= std_logic_vector(to_unsigned(6, 4));
  wait for 10 ns;
  num1 <= std_logic_vector(to_unsigned(5, 4));
  num2 <= std_logic_vector(to_unsigned(2, 4));
  wait for 10 ns;
  num1 <= std_logic_vector(to_unsigned(10, 4));
  num2 <= std_logic_vector(to_unsigned(8, 4));
  wait for 10 ns;


  -- for i in 0 to 15 loop
  --   for j in 0 to 15 loop
  --     A <= std_logic_vector(to_unsigned(i, 4));
  --     B <= std_logic_vector(to_unsigned(j, 4));
  --     wait for 10 ns;
  --   end loop;
  -- end loop;

  wait;
end process;
```

 سپس با انتخاب معماری آن در منوی waveform می توانیم شروع به ران کردن تست کنیم.



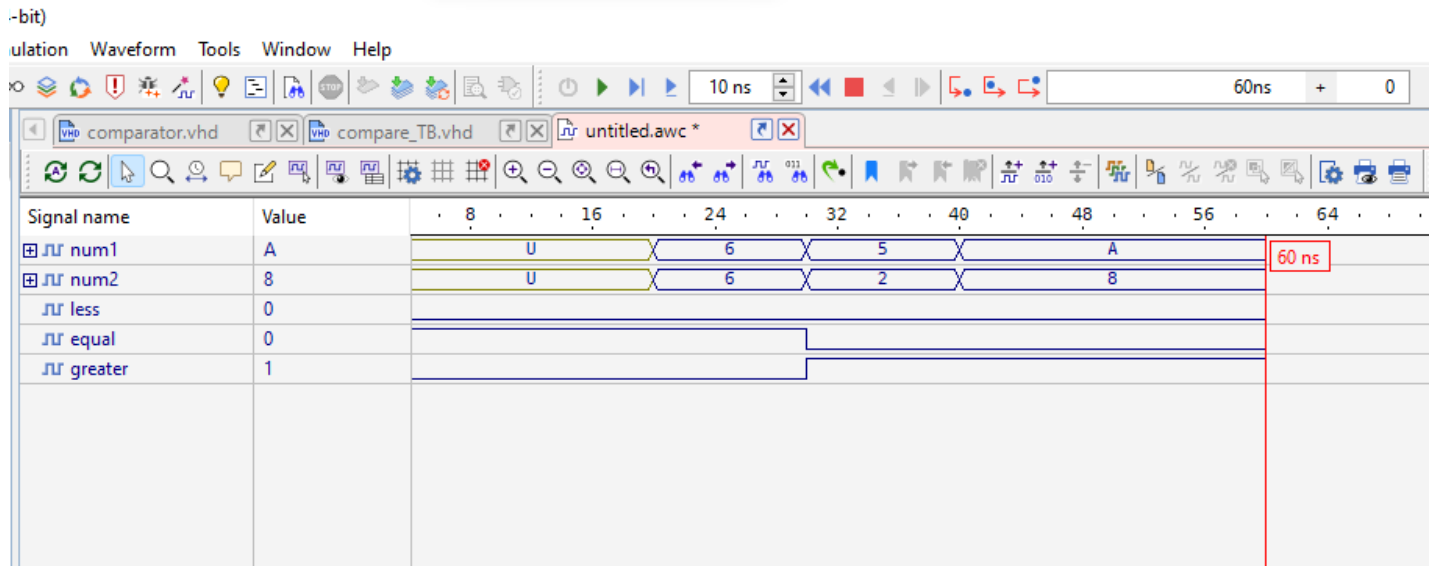
نمونه waveform ران شدن testbench برای سوال دوم:



سوال (3)

روند ایجاد پروژه و کد ها را مشابه سوال دوم انجام می دهیم.

تصویر شماتیک:

 


```

architecture Behavioral of ALU is
begin
  process(A, B, F_select, C_in)
    -- the result may have overflow . so we will use 8 bit variable for result
    variable temp_result: STD_LOGIC_VECTOR(8 downto 0);
    begin
      case F_select is
        when "000" =>
          -- A +1
          temp_result := ('0' & A) + 1;
          Y <= temp_result(7 downto 0);
        when "001" =>
          Y <= A + B;
        when "010" =>
          Y <= signed(A) + signed(B);
        when "011" =>
          temp_result := ('0' & A) + ('0' & B) + C_in;
          Y <= temp_result(7 downto 0);
        when "100" =>
          Y <= not A;
        when "101" =>
          Y <= not A + 1;
        when "110" =>
          Y <= A nand B;
        when "111" =>
          Y <= A xor B;
        when others =>
          Y <= (others => '0'); -- default case
      end case;
    end process;
  end Behavioral;

```


```

-- Add your stimulus here ...
process
begin
  -- Test each function in sequence
  -- Increment
  F_select <= "000"; A <= "00000001"; wait for 10 ns;
  -- Unsigned Add
  F_select <= "001"; A <= "00000010"; B <= "00000010"; wait for 10 ns;
  -- Signed Add
  F_select <= "010";
  F_select <= "001"; A <= "00000011"; B <= "10000010"; wait for 10 ns;
  -- Add with carry
  F_select <= "011"; A <= "00000100"; B <= "00000010";
  C_in <= '1'; wait for 10 ns;
  -- complement
  F_select <= "100"; A <= "00000001"; wait for 10 ns;
  -- 2's complement
  F_select <= "101"; A <= "00000001"; wait for 10 ns;
  -- NAND
  F_select <= "110"; A <= "00000010"; B <= "00000010"; wait for 10 ns;
  -- XOR
  F_select <= "111"; A <= "00000010"; B <= "00000010"; wait for 10 ns;

  wait;
end process;

```

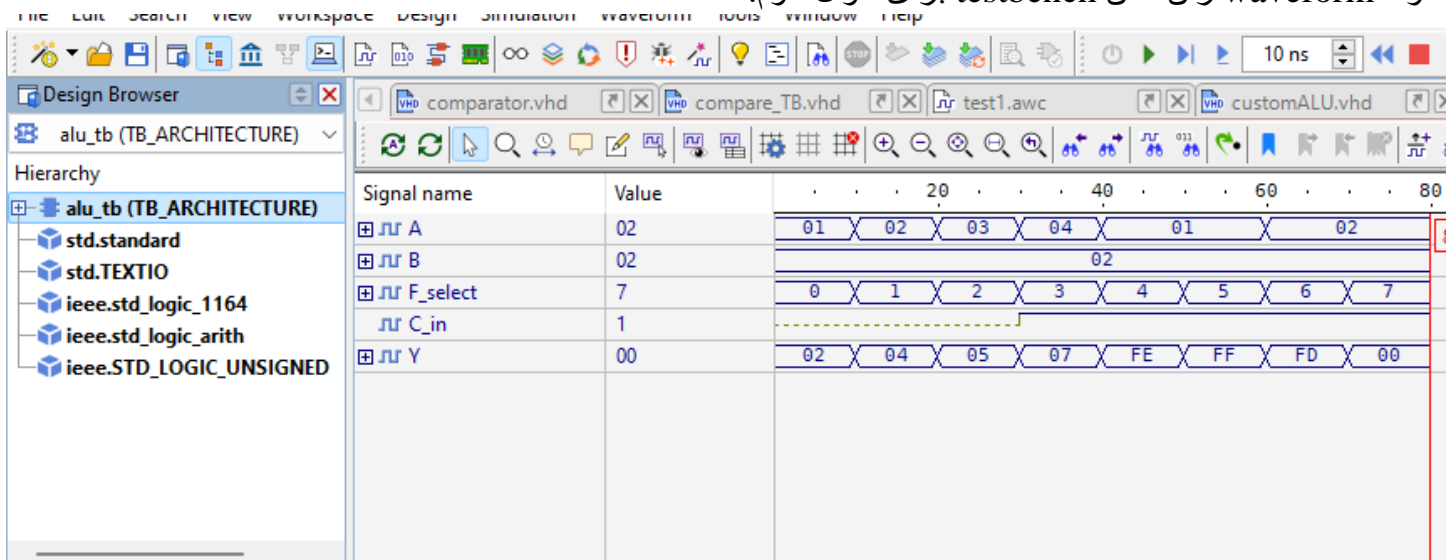نمونه waveform ران شدن testbench برای سوال سوم:



سوال (4)

پیاده سازی به روش when else:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity PriorityEncoder_OPERATORS is
    Port (
        inp : in std_logic_vector(6 downto 0);
        outp : out std_logic_vector(2 downto 0)
    );
end PriorityEncoder_OPERATORS;

architecture Behavioral of PriorityEncoder_OPERATORS is
begin
    outp <= "000" when inp = "0000000" else
            "001" when inp(0) = '1' else
            "010" when inp(1) = '1' else
            "011" when inp(2) = '1' else
            "100" when inp(3) = '1' else
            "101" when inp(4) = '1' else
            "110" when inp(5) = '1' else
            "111";
end Behavioral;
```

پیاده سازی با گیت های منطقی:


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity PriorityEncoder_gates is
    Port (
        inp : in std_logic_vector(6 downto 0);
        outp : out std_logic_vector(2 downto 0)
    );
end PriorityEncoder_gates;

architecture Behavioral_gates of PriorityEncoder_gates is
begin
    outp(0) <= inp(0) OR
        (NOT inp(0) AND NOT inp(1) AND inp(2)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND inp(4)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND NOT inp(4) AND NOT inp(5) AND inp(6));

    outp(1) <= (NOT inp(0) AND inp(1)) OR
        (NOT inp(0) AND NOT inp(1) AND inp(2)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND NOT inp(4) AND inp(5)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND NOT inp(4) AND NOT inp(5) AND inp(6));

    outp(2) <= (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND inp(3)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND inp(4)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND NOT inp(4) AND inp(5)) OR
        (NOT inp(0) AND NOT inp(1) AND NOT inp(2) AND NOT inp(3) AND NOT inp(4) AND NOT inp(5) AND inp(6));

end Behavioral_gates;

```

نمونه فایل testbench :

```

begin


    -- Unit Under Test port map
    UUT : priorityencoder_when_else
        port map (
            inp => inp,
            outp => outp
        );

    -- Add your stimulus here ...
process
begin
    -- Test all possible combinations
    for i in 0 to 127 loop
        inp <= std_logic_vector(to_unsigned(i, 7));
        wait for 10 ns;
    end loop;
    wait;
end process;

end TB_ARCHITECTURE;

```

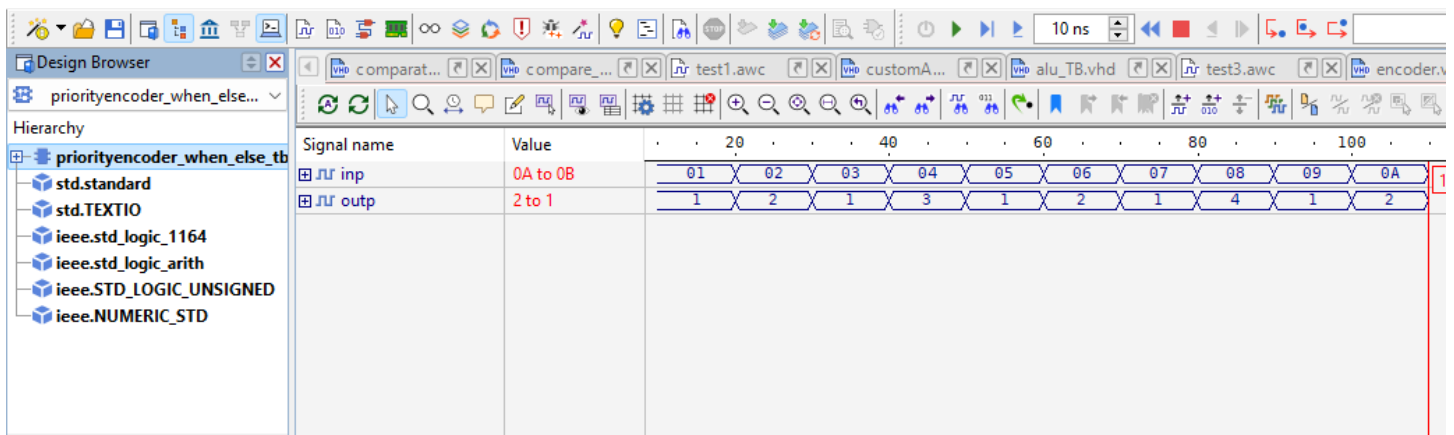نمونه های waveform را ن شدن testbench برای سوال چهارم:



Design Browser

priorityencoder_gates_tb (TB_AR...

Hierarchy

priorityencoder_gates_tb (TB_ARCHI

std.standard

std.TEXTIO

ieee.std_logic_1164

ieee.std_logic_arith

ieee.NUMERIC_STD

ne

inp

outp

Value

0A

2

comparator...

compare_T...

customALU...

encoder.vhd

priorityenc...

encoder_ga...

Signal name

Value

20

40

60

80

100

inp

0A

00

01

02

03

04

05

06

07

08

09

outp

2

0

1

2

1

3

1

2

1

4

1

	Value
inp	0A
outp	2

Signal name	Value	20		40		60		80		100	
Ⓜ inp	0A	00	01	02	03	04	05	06	07	08	09
Ⓜ outp	2	0	1	2	1	3	1	2	1	4	1